

ME 285 Fundamentals of Mechatronics

Hw #1: Introduction to Mechatronics and Basic Electronics (Due 1/31/01)

1. From the [May 1997 feature article in Mechanical Engineering magazine](http://www.memagazine.org/backissues/may97/features/mechtron/mechtron.html) (<http://www.memagazine.org/backissues/may97/features/mechtron/mechtron.html>) on mechatronics:
 - a. Why is Mechatronics important? Support your answer from information presented in the article.
 - b. What are the career opportunities like for mechanical engineers with training in mechatronics?
2. From the paper, “What is Mechatronics?”, by David Auslander,
 - a. How would you describe his view of what mechatronics is all about?
 - b. What are some of the major technological developments that have enabled mechatronics?
 - c. What are some of the key issues in computational software used for mechatronics systems?
3. The circuit schematic below shows a model of a data port (like the serial port on your computer) to which a load (modeled as a resistor, R_L) is connected
 - a. What is the output impedance of the port in terms of R_1 and R_2 ? (Hint: find the Thevinin equivalent circuit for the port)
 - b. What is the input impedance of the load in terms of R_L ?
 - c. Let $V_1=10$ V, $R_1=R_2=1$ k Ω . Plot V_A and the power dissipated by the load resistor R_L vs. the value of R_L using the range of R_L values listed. Use an engineering computation tool such as Excel, Matlab, etc. to generate your plot. Plot both curves on the same graph, and use a log scale for R_L (It is really easy to do in Excel. Just use the ‘Chart Wizard’, and Add data series. See me if you have questions on this). Please **explain** your observations about what happens to V_A and the power dissipated as a function of R_L .
 - d. If you wanted to make sure that V_A does not drop lower than 10% of its open-circuit value (i.e. the voltage when R_L is infinite), approximately what is the minimum value of R_L that you could use?
 - e. In summary then, what should you be careful about when you hook up a load (represented here by R_L) to a port or signal source?

